

VHDL

- In this lecture, we will go over examples of VHDL in comparison to SystemVerilog
- Examples taken from Ch. 4 of the Harris & Harris book 2nd Edition (recommended but not required book for this class)

Modules and Assign Statements

HDL Example 4.3 LOGIC GATES

SystemVerilog

```
module gates(input  logic [3:0] a, b,  
            output logic [3:0] y1, y2,  
                    y3, y4, y5);  
  
    /* five different two input logic  
       gates acting on 4 bit busses */  
    assign y1=a & b;    // AND  
    assign y2=a | b;    // OR  
    assign y3=a ^ b;    // XOR  
    assign y4=~(a & b); // NAND  
    assign y5=~(a | b); // NOR  
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;  
  
entity gates is  
    port(a, b: in  STD_LOGIC_VECTOR(3 downto 0);  
          y1, y2, y3, y4,  
          y5: out STD_LOGIC_VECTOR(3 downto 0));  
end;  
  
architecture synth of gates is  
begin  
    -- five different two input logic gates  
    -- acting on 4 bit busses  
    y1 <= a and b;  
    y2 <= a or b;  
    y3 <= a xor b;  
    y4 <= a nand b;  
    y5 <= a nor b;  
end;
```

 


Figure 4.4 gates synthesized circuit

Conditional Assignment

HDL Example 4.5 2:1 MULTIPLEXER

SystemVerilog

```
module mux2(input  logic [3:0] d0, d1,  
            input  logic    s,  
            output logic [3:0] y);  
  
    assign y = s ? d1 : d0;  
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;  
  
entity mux2 is  
    port(d0, d1: in  STD_LOGIC_VECTOR(3 downto 0);  
          s:      in  STD_LOGIC;  
          y:      out STD_LOGIC_VECTOR(3 downto 0));  
end;  
  
architecture synth of mux2 is  
begin  
    y <= d1 when s else d0;  
end;
```

 


Figure 4.6 mux2 synthesized circuit

More Assign Statements

HDL Example 4.7 FULL ADDER

SystemVerilog

```
module fulladder(input  logic a, b, cin,  
                 output logic s, cout);  
  
    logic p, g;  
  
    assign p = a ^ b;  
    assign g = a & b;  
  
    assign s = p ^ cin;  
    assign cout = g | (p & cin);  
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;  
  
entity fulladder is  
    port(a, b, cin: in  STD_LOGIC;  
          s, cout: out STD_LOGIC);  
end;  
  
architecture synth of fulladder is  
    signal p, g: STD_LOGIC;  
begin  
    p <= a xor b;  
    g <= a and b;  
  
    s <= p xor cin;  
    cout <= g or (p and cin);  
end;
```

 


Figure 4.8 fulladder synthesized circuit

Operators

HDL Example 4.8 OPERATOR PRECEDENCE

SystemVerilog

Table 4.1 SystemVerilog operator precedence

	Op	Meaning
H i g h e s t	~	NOT
	*, /, %	MUL, DIV, MOD
	+, -	PLUS, MINUS
	<<, >>	Logical Left/Right Shift
	<<<, >>>	Arithmetic Left/Right Shift
	<, <=, >, >=	Relative Comparison
L o w e s t	==, !=	Equality Comparison
	&, ~&	AND, NAND
	^, ~^	XOR, XNOR
	, ~	OR, NOR
	?:	Conditional

VHDL

Table 4.2 VHDL operator precedence

	Op	Meaning
H i g h e s t	not	NOT
	*, /, mod, rem	MUL, DIV, MOD, REM
	+, -	PLUS, MINUS
	rol, ror, srl, sll	Rotate, Shift logical
	<, <=, >, >=	Relative Comparison
	=, /=	Equality Comparison
L o w e s t	and, or, nand, nor, xor, xnor	Logical Operations

L
.

Numbers

HDL Example 4.9 NUMBERS

SystemVerilog

Table 4.3 SystemVerilog numbers

Numbers	Bits	Base	Val	Stored
3'b101	3	2	5	101
'b11	?	2	3	000 ... 0011
8'b11	8	2	3	00000011
8'b1010_1011	8	2	171	10101011
3'd6	3	10	6	110
6'o42	6	8	34	100010
8'hAB	8	16	171	10101011
42	?	10	42	00 ... 0101010

VHDL

Table 4.4 VHDL numbers

Numbers	Bits	Base	Val	Stored
3B"101"	3	2	5	101
B"11"	2	2	3	11
8B"11"	8	2	3	00000011
8B"1010_1011"	8	2	171	10101011
3D"6"	3	10	6	110
6O"42"	6	8	34	100010
8X"AB"	8	16	171	10101011
"101"	3	2	5	101
B"101"	3	2	5	101
X"AB"	8	16	171	10101011

Bit Manipulations

HDL Example 4.12 BIT SWIZZLING

SystemVerilog

```
assign y = {c[2:1], {3{d[0]}}, c[0], 3'b101};
```

VHDL

```
y <= (c(2 downto 1), d(0), d(0), d(0), c(0), 3B"101");
```

Module Instantiations

HDL Example 4.14 STRUCTURAL MODEL OF 4:1 MULTIPLEXER

SystemVerilog

```
module mux4(input  logic [3:0] d0, d1, d2, d3,  
            input  logic [1:0] s,  
            output logic [3:0] y);  
  
    logic [3:0] low, high;  
  
    mux2 lowmux(d0, d1, s[0], low);  
    mux2 highmux(d2, d3, s[0], high);  
    mux2 finalmux(low, high, s[1], y);  
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;  
  
entity mux4 is  
    port(d0, d1,  
          d2, d3: in  STD_LOGIC_VECTOR(3 downto 0);  
          s:   in  STD_LOGIC_VECTOR(1 downto 0);  
          y:   out STD_LOGIC_VECTOR(3 downto 0));  
end;  
  
architecture struct of mux4 is  
    component mux2  
        port(d0,  
              d1: in  STD_LOGIC_VECTOR(3 downto 0);  
              s: in  STD_LOGIC;  
              y: out STD_LOGIC_VECTOR(3 downto 0));  
    end component;  
    signal low, high: STD_LOGIC_VECTOR(3 downto 0);  
begin  
    lowmux:  mux2 port map(d0, d1, s(0), low);  
    highmux: mux2 port map(d2, d3, s(0), high);  
    finalmux: mux2 port map(low, high, s(1), y);  
end;
```

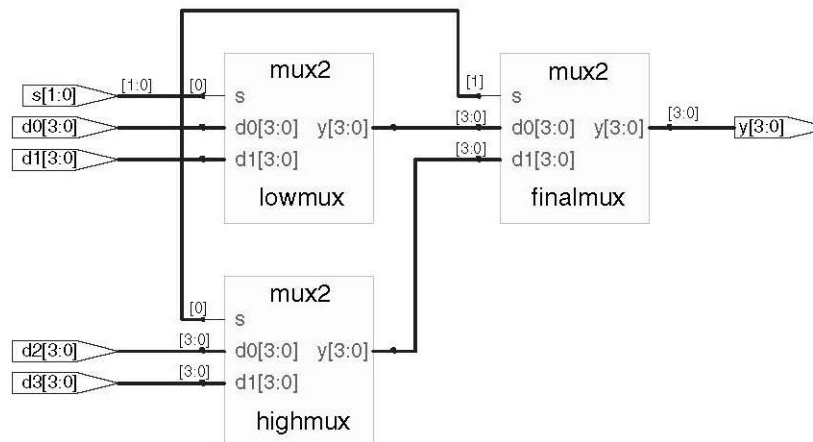


Figure 4.11 mux4 synthesized circuit

Module Instantiations

HDL Example 4.16 ACCESSING PARTS OF BUSSES

SystemVerilog

```
module mux2_8(input  logic [7:0] d0, d1,  
             input  logic      s,  
             output logic [7:0] y);  
  
    mux2 lsbmux(d0[3:0], d1[3:0], s, y[3:0]);  
    mux2 msbmux(d0[7:4], d1[7:4], s, y[7:4]);  
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;  
entity mux2_8 is  
    port(d0, d1: in  STD_LOGIC_VECTOR(7 downto 0);  
          s:      in  STD_LOGIC;  
          y:      out STD_LOGIC_VECTOR(7 downto 0));  
end;  
architecture struct of mux2_8 is  
    component mux2  
        port(d0, d1: in  STD_LOGIC_VECTOR(3 downto 0);  
              s:      in  STD_LOGIC;  
              y:      out STD_LOGIC_VECTOR(3 downto 0));  
    end component;  
begin  
    lsbmux: mux2  
        port map(d0(3 downto 0), d1(3 downto 0),  
                  s, y(3 downto 0));  
    msbmux: mux2  
        port map(d0(7 downto 4), d1(7 downto 4),  
                  s, y(7 downto 4));  
end;
```

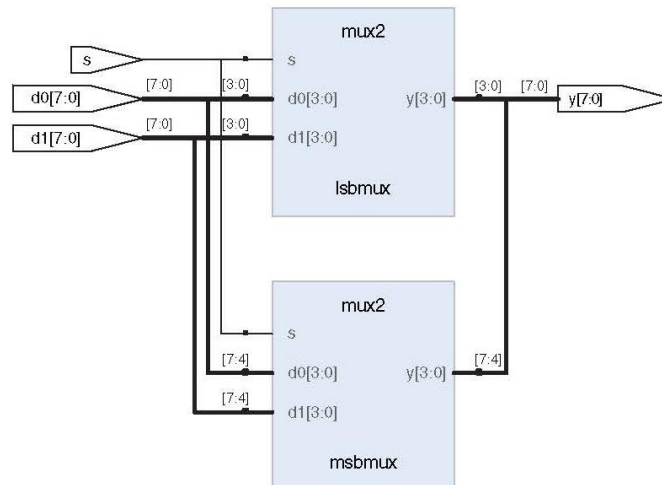


Figure 4.13 mux2_8 synthesized circuit

Register

HDL Example 4.17 REGISTER

SystemVerilog

```
module flop(input  logic    clk,  
            input  logic [3:0] d,  
            output logic [3:0] q);  
  
    always_ff @(posedge clk)  
        q <= d;  
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;  
entity flop is  
    port(clk: in  STD_LOGIC;  
          d:  in  STD_LOGIC_VECTOR(3 downto 0);  
          q:  out STD_LOGIC_VECTOR(3 downto 0));  
end;  
architecture synth of flop is  
begin  
    process(clk) begin  
        if rising_edge(clk) then  
            q <= d;  
        end if;  
    end process;  
end;
```



Figure 4.14 flop synthesized circuit

Resettable Register

HDL Example 4.18 RESETTABLE REGISTER


SystemVerilog

```
module flopr(input logic clk,
            input logic reset,
            input logic [3:0] d,
            output logic [3:0] q);

// asynchronous reset
always_ff @(posedge clk, posedge reset)
    if (reset) q <= 4'b0;
    else q <= d;
endmodule

module flopr(input logic clk,
            input logic reset,
            input logic [3:0] d,
            output logic [3:0] q);

 // synchronous reset
always_ff @(posedge clk)
    if (reset) q <= 4'b0;
    else q <= d;
endmodule
```



(a)



(b)

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity flopr is
    port(clk, reset: in STD_LOGIC;
         d: in STD_LOGIC_VECTOR(3 downto 0);
         q: out STD_LOGIC_VECTOR(3 downto 0));
end;

architecture asynchronous of flopr is
begin
    process(clk, reset) begin
        if reset then
            q <= "0000";
        elsif rising_edge(clk) then
            q <= d;
        end if;
    end process;
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity flopr is
    port(clk, reset: in STD_LOGIC;
         d: in STD_LOGIC_VECTOR(3 downto 0);
         q: out STD_LOGIC_VECTOR(3 downto 0));
end;

architecture synchronous of flopr is
begin
    process(clk) begin
        if rising_edge(clk) then
            if reset then q <= "0000";
            else q <= d;
            end if;
        end if;
    end process;
end;
```

Figure 4.15 flopr synthesized circuit (a) asynchronous reset, (b) synchronous reset

Resettable Enabled Register

HDL Example 4.19 RESETTABLE ENABLED REGISTER

SystemVerilog

```
module flopenr(input logic clk,
               input logic reset,
               input logic en,
               input logic [3:0] d,
               output logic [3:0] q);

// asynchronous reset
always_ff@(posedge clk, posedge reset)
    if (reset) q <= 4'b0;
    else if (en) q <= d;
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
entity flopenr is
    port(clk,
          reset,
          en: in STD_LOGIC;
          d: in STD_LOGIC_VECTOR(3 downto 0);
          q: out STD_LOGIC_VECTOR(3 downto 0));
end;
architecture asynchronous of flopenr is
    -- asynchronous reset
    begin
        process(clk, reset) begin
            if reset then
                q <= "0000";
            elsif rising_edge(clk) then
                if en then
                    q <= d;
                end if;
            end if;
        end process;
    end;
```

 


Figure 4.16 flopenr synthesized circuit

Multiple Registers

HDL Example 4.20 SYNCHRONIZER

SystemVerilog

```
module sync(input  logic clk,
            input  logic d,
            output logic q);

  logic n1;

  always_ff@(posedge clk)
  begin
    n1 <= d; // nonblocking
    q <= n1; // nonblocking
  end
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity sync is
  port(clk: in  STD_LOGIC;
        d:  in  STD_LOGIC;
        q:  out STD_LOGIC);
end;

architecture good of sync is
  signal n1: STD_LOGIC;
begin
  process(clk) begin
    if rising_edge(clk) then
      n1 <= d;
      q <= n1;
    end if;
  end process;
end;
```

 


Figure 4.18 sync synthesized circuit

Always Comb

HDL Example 4.23 FULL ADDER USING always/process

SystemVerilog

```
module fulladder(input  logic a, b, cin,
                 output logic s, cout);
    logic p, g;
    always_comb
    begin
        p=a ^ b;           // blocking
        g=a & b;           // blocking
        s=p ^ cin;         // blocking
        cout=g | (p & cin); // blocking
    end
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
entity fulladder is
    port(a, b, cin: in  STD_LOGIC;
          s, cout:  out STD_LOGIC);
end;
architecture synth of fulladder is
begin
    process(all)
        variable p, g: STD_LOGIC;
    begin
        p := a xor b; -- blocking
        g := a and b; -- blocking
        s <= p xor cin;
        cout <= g or (p and cin);
    end process;
end;
```


Case Statement

HDL Example 4.24 SEVEN-SEGMENT DISPLAY DECODER

SystemVerilog

```
module sevenseg(input  logic [3:0] data,
               output logic [6:0] segments);
  always_comb
  case(data)
    //      abc_defg
    0:      segments = 7'b111_1110;
    1:      segments = 7'b011_0000;
    2:      segments = 7'b110_1101;
    3:      segments = 7'b111_1001;
    4:      segments = 7'b011_0011;
    5:      segments = 7'b101_1011;
    6:      segments = 7'b101_1111;
    7:      segments = 7'b111_0000;
    8:      segments = 7'b111_1111;
    9:      segments = 7'b111_0011;
    default: segments = 7'b000_0000;
  endcase
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
entity seven_seg_decoder is
  port(data:   in  STD_LOGIC_VECTOR(3 downto 0);
        segments: out STD_LOGIC_VECTOR(6 downto 0));
end;
architecture synth of seven_seg_decoder is
begin
  process(all) begin
    case data is
      --      abcdefg
      when X"0" => segments <= "1111110";
      when X"1" => segments <= "0110000";
      when X"2" => segments <= "1101101";
      when X"3" => segments <= "1111001";
      when X"4" => segments <= "0110011";
      when X"5" => segments <= "1011011";
      when X"6" => segments <= "1011111";
      when X"7" => segments <= "1110000";
      when X"8" => segments <= "1111111";
      when X"9" => segments <= "1110011";
      when others => segments <= "0000000";
    end case;
  end process;
end;
```



Figure 4.20 sevenseg synthesized circuit

Case Statement

HDL Example 4.25 3:8 DECODER

SystemVerilog

```
module decoder3_8(input  logic [2:0] a,
                 output logic [7:0] y);
    always_comb
    case(a)
        3'b000: y = 8'b00000001;
        3'b001: y = 8'b00000010;
        3'b010: y = 8'b00000100;
        3'b011: y = 8'b00001000;
        3'b100: y = 8'b00010000;
        3'b101: y = 8'b00100000;
        3'b110: y = 8'b01000000;
        3'b111: y = 8'b10000000;
        default: y = 8'bxxxxxxxx;
    endcase
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
entity decoder3_8 is
    port(a: in  STD_LOGIC_VECTOR(2 downto 0);
         y: out STD_LOGIC_VECTOR(7 downto 0));
end;
architecture synth of decoder3_8 is
begin
    process(all) begin
        case a is
            when "000" => y <= "00000001";
            when "001" => y <= "00000010";
            when "010" => y <= "00000100";
            when "011" => y <= "00001000";
            when "100" => y <= "00010000";
            when "101" => y <= "00100000";
            when "110" => y <= "01000000";
            when "111" => y <= "10000000";
            when others => y <= "XXXXXXXX";
        end case;
    end process;
end;
```

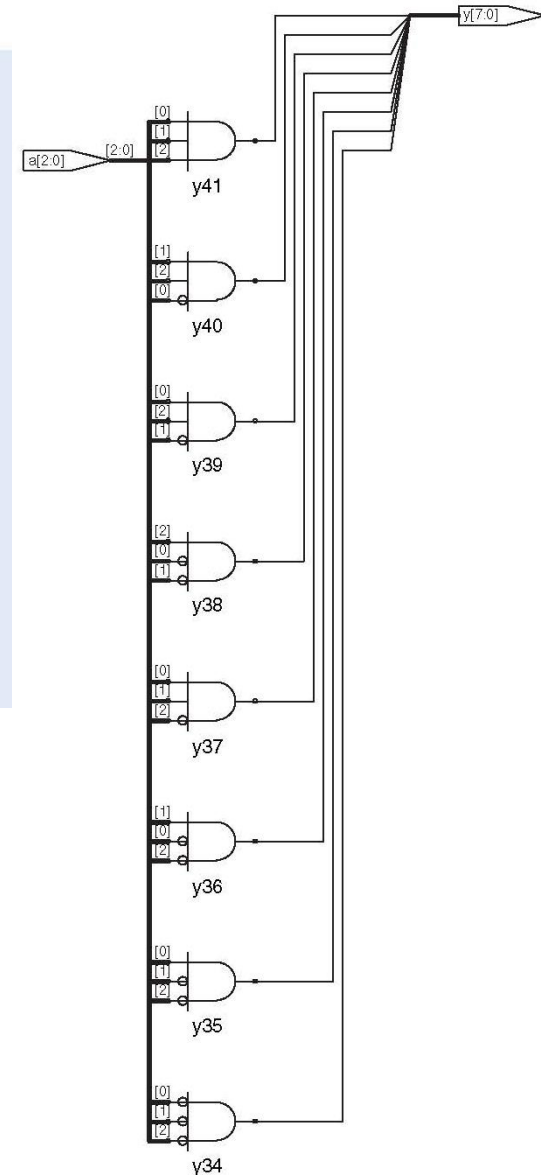


Figure 4.21 decoder3_8 synthesized circuit

More If-Then-Else

HDL Example 4.26 PRIORITY CIRCUIT

SystemVerilog

```
module priorityckt(input  logic [3:0] a,  
                  output logic [3:0] y);  
  
  always_comb  
  if      (a[3]) y <= 4'b1000;  
  else if (a[2]) y <= 4'b0100;  
  else if (a[1]) y <= 4'b0010;  
  else if (a[0]) y <= 4'b0001;  
  else          y <= 4'b0000;  
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;  
entity priorityckt is  
  port(a: in  STD_LOGIC_VECTOR(3 downto 0);  
        y: out STD_LOGIC_VECTOR(3 downto 0));  
end;  
  
architecture synth of priorityckt is  
begin  
  process(a11) begin  
    if  a(3) then y <= "1000";  
    elsif a(2) then y <= "0100";  
    elsif a(1) then y <= "0010";  
    elsif a(0) then y <= "0001";  
    else          y <= "0000";  
    end if;  
  end process;  
end;
```

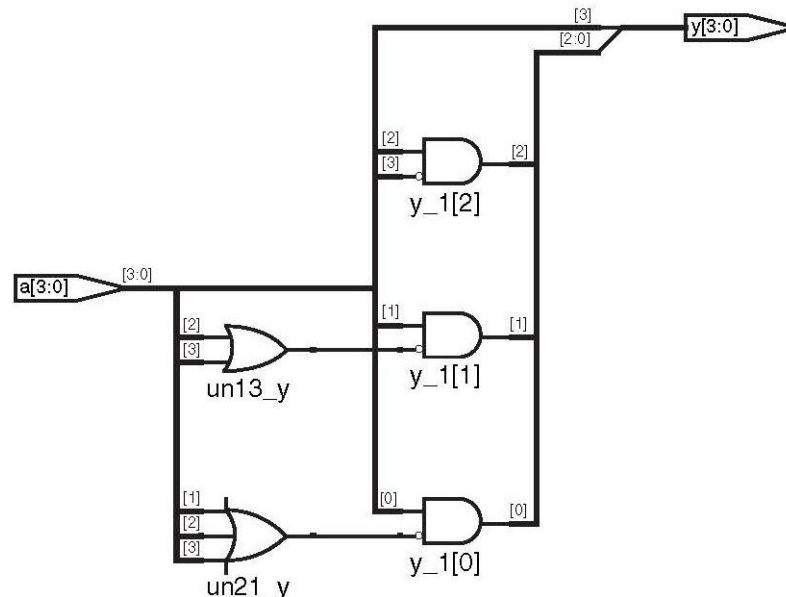


Figure 4.22 priorityckt synthesized circuit

Casez Statement

HDL Example 4.27 PRIORITY CIRCUIT USING DON'T CARES

SystemVerilog

```
module priority_casex(input  logic [3:0] a,  
                    output logic [3:0] y);  
  
    always_comb  
    casez(a)  
        4'b1??? : y <= 4'b1000;  
        4'b01?? : y <= 4'b0100;  
        4'b001? : y <= 4'b0010;  
        4'b0001 : y <= 4'b0001;  
        default : y <= 4'b0000;  
    endcase  
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;  
  
entity priority_casex is  
    port(a: in  STD_LOGIC_VECTOR(3 downto 0);  
         y: out STD_LOGIC_VECTOR(3 downto 0));  
end;  
  
architecture dontcare of priority_casex is  
begin  
    process(all) begin  
        case? a is  
            when "1---" => y <= "1000";  
            when "01--" => y <= "0100";  
            when "001-" => y <= "0010";  
            when "0001" => y <= "0001";  
            when others => y <= "0000";  
        end case?;  
    end process;  
end;
```

 


Figure 4.23 priority_casex synthesized circuit

Blocking vs. Non-Blocking

BLOCKING AND NONBLOCKING ASSIGNMENT GUIDELINES

SystemVerilog

1. Use `always_ff @(posedge clk)` and nonblocking assignments to model synchronous sequential logic.

```
always_ff @(posedge clk)
begin
    n1 <= d; // nonblocking
    q <= n1; // nonblocking
end
```

2. Use continuous assignments to model simple combinational logic.

```
assign y = s ? d1 : d0;
```

3. Use `always_comb` and blocking assignments to model more complicated combinational logic where the `always` statement is helpful.

```
always_comb
begin
    p = a ^ b; // blocking
    g = a & b; // blocking
    s = p ^ cin;
    cout = g | (p & cin);
end
```

4. Do not make assignments to the same signal in more than one `always` statement or continuous assignment statement.

VHDL

1. Use `process(clk)` and nonblocking assignments to model synchronous sequential logic.

```
process(clk) begin
    if rising_edge(clk) then
        n1 <= d; -- nonblocking
        q <= n1; -- nonblocking
    end if;
end process;
```

2. Use concurrent assignments outside `process` statements to model simple combinational logic.

```
y <= d0 when s = '0' else d1;
```

3. Use `process(all)` to model more complicated combinational logic where the process is helpful. Use blocking assignments for internal variables.

```
process(all)
    variable p, g: STD_LOGIC;
begin
    p := a xor b; -- blocking
    g := a and b; -- blocking
    s <= p xor cin;
    cout <= g or (p and cin);
end process;
```

4. Do not make assignments to the same variable in more than one process or concurrent assignment statement.

Finite State Machine

HDL Example 4.31 PATTERN RECOGNIZER MOORE FSM

SystemVerilog

```
module patternMoore(input  logic clk,
                   input  logic reset,
                   input  logic a,
                   output logic y);

  typedef enum logic [1:0] {S0, S1, S2} statetype;
  statetype state, nextstate;

  // state register
  always_ff @(posedge clk, posedge reset)
    if (reset) state <= S0;
    else      state <= nextstate;

  // next state logic
  always_comb
    case (state)
      S0: if (a) nextstate=S0;
          else nextstate=S1;
      S1: if (a) nextstate=S2;
          else nextstate=S1;
      S2: if (a) nextstate=S0;
          else nextstate=S1;
      default: nextstate=S0;
    endcase

  // output logic
  assign y=(state==S2);
endmodule
```

 


Figure 4.26 patternMoore synthesized circuit

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity patternMoore is
  port(clk, reset: in  STD_LOGIC;
       a:      in  STD_LOGIC;
       y:      out STD_LOGIC);
end;

architecture synth of patternMoore is
  type statetype is (S0, S1, S2);
  signal state, nextstate: statetype;
begin
  -- state register
  process(clk, reset) begin
    if reset then
      state <= S0;
    elsif rising_edge(clk) then state <= nextstate;
    end if;
  end process;

  -- next state logic
  process(all) begin
    case state is
      when S0 =>
        if a then nextstate <= S0;
        else      nextstate <= S1;
        end if;
      when S1 =>
        if a then nextstate <= S2;
        else      nextstate <= S1;
        end if;
      when S2 =>
        if a then nextstate <= S0;
        else      nextstate <= S1;
        end if;
      when others =>
        nextstate <= S0;
    end case;
  end process;

  output logic
  y <= '1' when state=S2 else '0';
end;
```


Parameterized Modules

HDL Example 4.34 PARAMETERIZED N-BIT 2:1 MULTIPLEXERS

SystemVerilog

```
module mux2
  #(parameter width=8)
  (input  logic [width 1:0] d0, d1,
   input  logic           s,
   output logic [width 1:0] y);
  assign y = s ? d1 : d0;
endmodule

module mux4_8(input  logic [7:0] d0, d1, d2, d3,
             input  logic [1:0] s,
             output logic [7:0] y);

  logic [7:0] low, hi;

  mux2 lowmux(d0, d1, s[0], low);
  mux2 himux(d2, d3, s[0], hi);
  mux2 outmux(low, hi, s[1], y);
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity mux2 is
  generic(width: integer := 8);
  port(d0,
       d1: in  STD_LOGIC_VECTOR(width 1 downto 0);
       s: in  STD_LOGIC;
       y: out STD_LOGIC_VECTOR(width 1 downto 0));
end;

architecture synth of mux2 is
begin
  y <= d1 when s else d0;
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity mux4_8 is
  port(d0, d1, d2,
       d3: in  STD_LOGIC_VECTOR(7 downto 0);
       s: in  STD_LOGIC_VECTOR(1 downto 0);
       y: out STD_LOGIC_VECTOR(7 downto 0));
end;

architecture struct of mux4_8 is
  component mux2
    generic(width: integer := 8);
    port(d0,
         d1: in  STD_LOGIC_VECTOR(width 1 downto 0);
         s: in  STD_LOGIC;
         y: out STD_LOGIC_VECTOR(width 1 downto 0));
  end component;
  signal low, hi: STD_LOGIC_VECTOR(7 downto 0);
begin
  lowmux: mux2 port map(d0, d1, s(0), low);
  himux:  mux2 port map(d2, d3, s(0), hi);
  outmux: mux2 port map(low, hi, s(1), y);
end;
```

Parameterized Modules

HDL Example 4.34 PARAMETERIZED N-BIT 2:1 MULTIPLEXERS

SystemVerilog

```
module mux4_12(input logic [11:0] d0, d1, d2, d3,  
              input logic [1:0] s,  
              output logic [11:0] y);  
  
    logic [11:0] low, hi;  
  
    mux2 #(12) lowmux(d0, d1, s[0], low);  
    mux2 #(12) himux(d2, d3, s[0], hi);  
    mux2 #(12) outmux(low, hi, s[1], y);  
endmodule
```

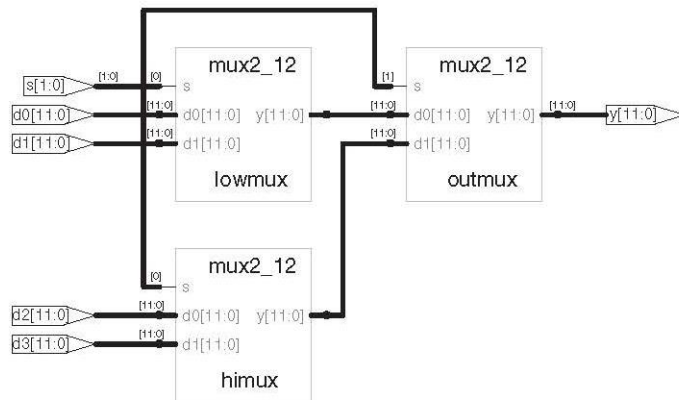


Figure 4.29 mux4_12 synthesized circuit

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;  
  
entity mux4_12 is  
    port(d0, d1, d2,  
          d3: in STD_LOGIC_VECTOR(7 downto 0);  
          s: in STD_LOGIC_VECTOR(1 downto 0);  
          y: out STD_LOGIC_VECTOR(7 downto 0));  
end;  
  
architecture struct of mux4_12 is  
    component mux2  
        generic(width: integer := 8);  
        port(d0,  
              d1: in STD_LOGIC_VECTOR(width 1 downto 0);  
              s: in STD_LOGIC;  
              y: out STD_LOGIC_VECTOR(width 1 downto 0));  
    end component;  
    signal low, hi: STD_LOGIC_VECTOR(7 downto 0);  
begin  
    lowmux: mux2 generic map(12)  
        port map(d0, d1, s(0), low);  
    himux: mux2 generic map(12)  
        port map(d2, d3, s(0), hi);  
    outmux: mux2 generic map(12)  
        port map(low, hi, s(1), y);  
end;
```