

Lecture 4


Chapter 2

- Kirchoff's ~~Circuit~~ ^{current} Law (KCL) } § 2.1-2.3
- Kirchoff's voltage Law (KVL) } pp. 53-89


In last Chapter, we introduced basic electrical quantities (current and voltage) and their relationship with electrical power and energy; we also learned basic circuit elements: sources and resistance. To analyze circuits, we still have to know fundamental laws that govern the behavior of voltages and currents in a circuit. This is what we are going to learn today. There are two fundamental laws, one governs the current; the other dictates the voltage. Before introducing the two laws, we first get to know some new terminology.

Some New Terminology

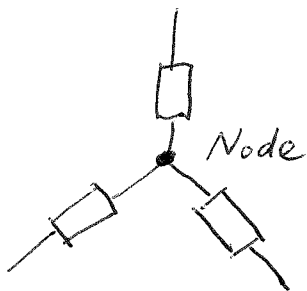- Node: the connection point of one or more circuit elements



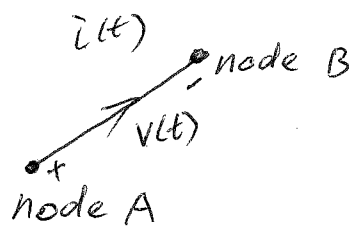
- Branch: symbolically, a line segment connecting two nodes.



It represents a generic two-terminal circuit element.

- Series circuit:

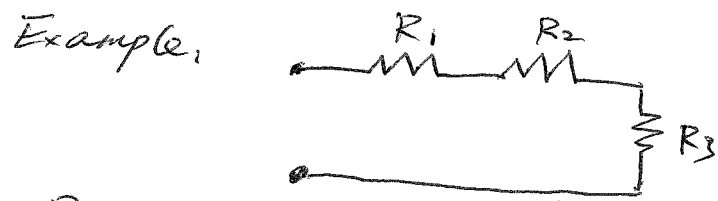
A sequential connection of 2-terminal circuit elements end to end.



- Parallel circuit:

Two-terminal circuit elements share both terminals in common. In other words, one terminal is wired together; the other is also wired together.

Example:

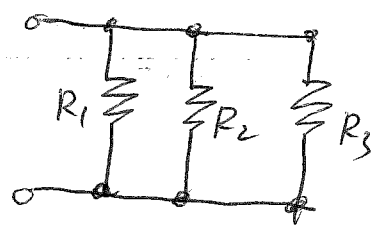

Kirchhoff's current Law (KCL)


■ The algebraic sum of the current entering (or leaving) a node is zero for every instant of time.

Mathematically written as

$$\sum I_{in} = 0$$
 OR

$$\sum I_{out} = 0$$

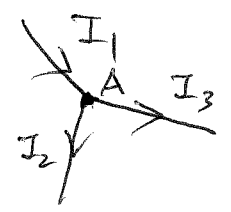• The above law can be understood in the following way.



Consider current I_1 entering node A. Imagine, this means a group of ~~electrons~~ ^{charges} flow into node A. Due to charge conservation, the same amount of charges will leave node A via path 2 and path 3. As a result,

$$I_1 = I_2 + I_3$$


Hence, $\overset{\text{Current entering node A from path 1}}{\circlearrowleft I_1} - \overset{\text{Current entering node A from path 2}}{\circlearrowright I_2} - \overset{\text{Current entering node A from path 3}}{\circlearrowright I_3} = 0 \implies \sum I_{in} = 0$

Similarly, $(-I_1) + I_2 + I_3 = 0$

Current leaving node A from path 1 Current leaving node A from path 2 Current leaving node A from path 3

i. e. the algebraic sum of the current leaving a node is also zero for every instant of time.

Example 1

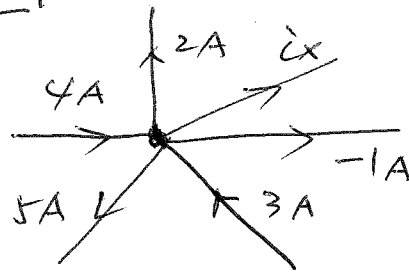


Find i_x .

Solution

$$\sum I_{in} = 0$$


$$4 - 2 + 1 - 5 + 3 - i_x = 0 \quad (1)$$

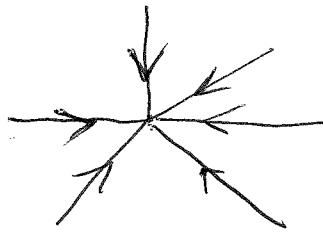The above is written by setting the reference direction of each branch as the direction entering the circuit node, i.e.



If the actual current given in the original problem agrees with the reference direction in that specific branch, then use that current as it is; otherwise, put '-' sign in front of the current.

From (1) $i_x = 1 \text{ (A)}$

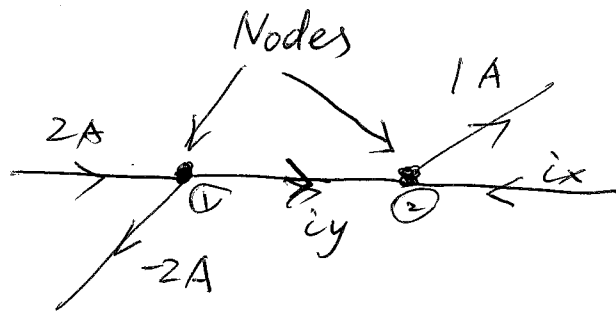Example 2

Find i_x

Solution At node ①, using KCL

$$2 - (-2) - i_y = 0$$

$$\Rightarrow i_y = 4 \text{ (A)}$$

At node ②, using KCL

$$i_x + i_y - 1 = 0$$


$$i_x = 1 - i_y = \boxed{-3} \text{ (A)}$$

▣ KCL is also valid for Gaussian curves (surfaces)

What are Gaussian curves (surfaces)?


They are "closed" curves (surfaces).

Example

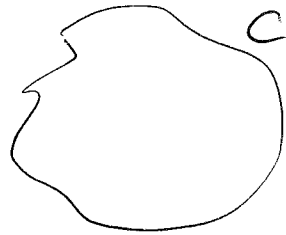

For the above closed contour C.

KCL also holds true. So

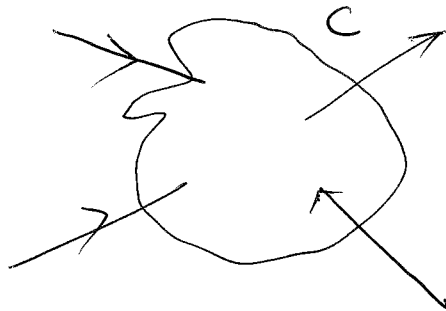


$$\sum I_{in} = 0$$

or $\sum I_{out} = 0$

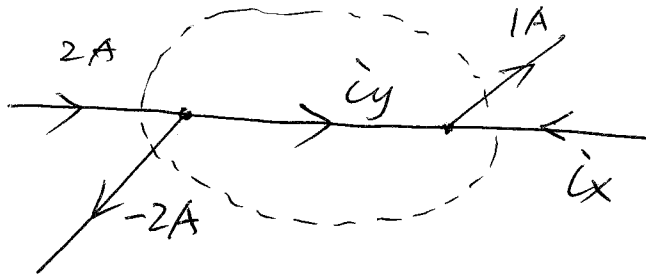(8)

We can resolve Example 2 by using the concept of Gaussian curves (surfaces)



Dashed line denotes a closed curve.

We apply KCL on this closed curve

$$\sum I_{in} = 0$$


$$\Rightarrow 2 - (-2) - 1 + i_x = 0$$

$$\Rightarrow 4 - 1 + i_x = 0$$

$$\Rightarrow \boxed{i_x = -3} \text{ (A)}$$

Same answer as we got by using node-based KCL.

Example 4 Find i_x

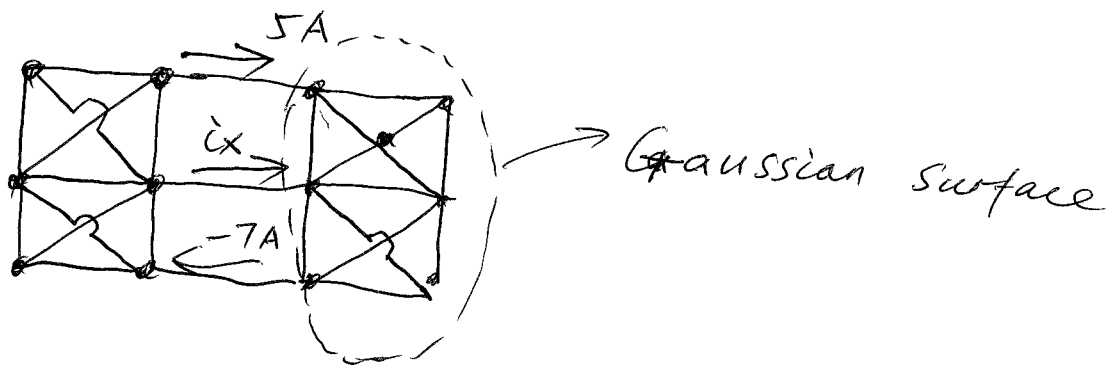

$$\sum I_{in} = 0$$

$$\Rightarrow i_x + 5 - (-7) = 0$$

$$\Rightarrow i_x = -12 \quad (A)$$

Kirchhoff's Voltage Law (KVL)


The algebraic sum of the voltage drops around any closed path (or closed node sequence) is zero at every instant of time.

$$\sum V_{drop} = 0$$

Definition:

- Closed path: a connection of circuit elements that ends and begins ~~at~~ at the same node, and traverse each node only once.
- Closed node sequence: A finite sequence of nodes that begins and ends at the same node.

Example:

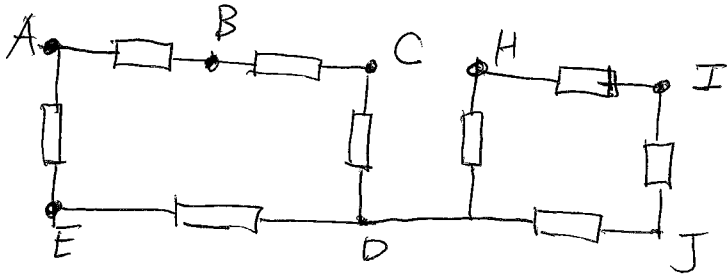

Closed path: $A \rightarrow B \rightarrow C \rightarrow D \rightarrow E$, $H \rightarrow I \rightarrow J \rightarrow D$

Closed node sequence: $ABCHIDEA$, $ABCHDEA$

- For any pair of nodes j and k , the voltage drop V_{jk} from node j to node k is

$$V_{jk} = V_j - V_k$$

V_j : electric potential at node j

also known as the voltage at node j
with respect to reference, since

$$V_j = V_j - 0$$

$$= V_j - V_{\text{ref}} \rightarrow \text{reference point (node)}$$

where potential is zero

The reference node is usually called 'ground'

Similarly,

V_k : node voltage at node k , i.e. the

voltage drop from node k to a reference node.

- Now, it is not difficult to understand KVL.


Take any closed node sequence as an example, say $ABCHDEA$

$$\begin{aligned} \sum V_{\text{drop}} &= V_{AB} + V_{BC} + V_{CH} + V_{HD} + V_{DE} + V_{EA} \\ &= V_A - V_B + V_B - V_C + V_C - V_H + \dots - V_E + V_E - V_A \\ &= 0 \end{aligned}$$

* You can also make an analogy between KVL and the gravitational potential drops around any closed path.

For example, you climb a mountain starting from a point at the foot of the hill, get to the top of the hill, then return to your starting point. The gravitational potential difference is zero although you went through a long and difficult path, because the path is closed.

Example Find V_x and i_x

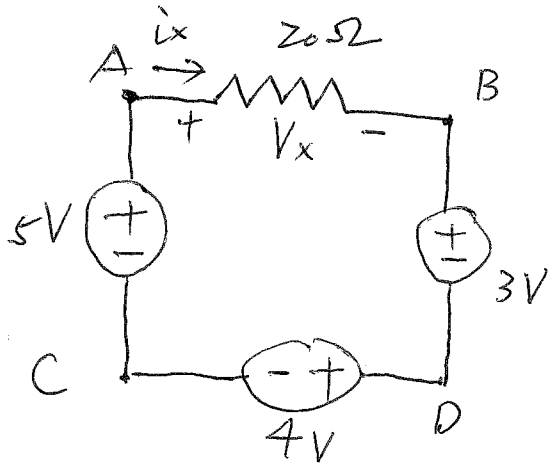

Solution Here, ~~ABDC~~ $A \rightarrow B \rightarrow D \rightarrow C$ is clearly a closed path.

We can apply KVL onto this path.

$$V_{AB} + V_{BD} + V_{DC} + V_{CA} = 0$$

$$V_x + 3 + 4 - 5 = 0$$

$$\Rightarrow V_x = 5 - 4 - 3 = -2 \text{ (V)}$$

$$i_x = \frac{V_x}{R} = \frac{-2}{20} = -0.1 \text{ (A)}$$


You can also use a reversed direction to calculate voltage drop, i.e. $A \rightarrow C \rightarrow D \rightarrow B$ (counter-clockwise)

then $V_{AC} + V_{CD} + V_{DB} + V_{BA} = 0$

$$\Rightarrow 5 + (-4) + (-3) + (-V_x) = 0$$

$$\Rightarrow V_x = -2 \text{ (V)} \quad \text{the same answer}$$

Example What is V_{BC} ?

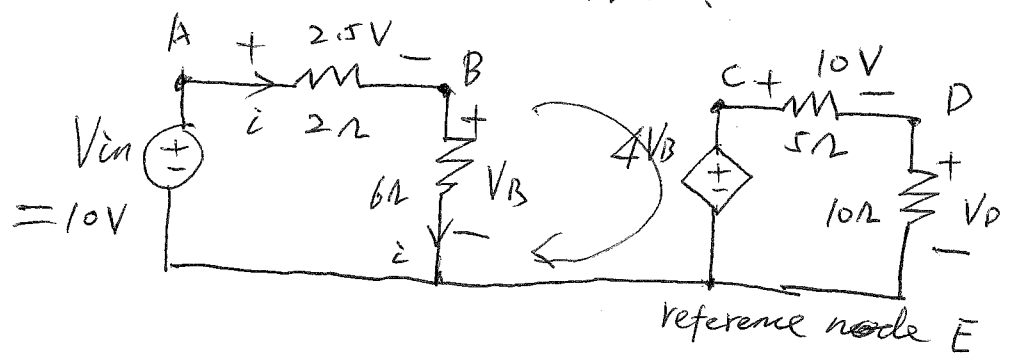

Solution BCEB is certainly a closed-node sequence, There are also many others such as ABCEA, ABCDEA. You can choose any of them to figure out V_{BC} . Let's use BCEB as an example.

$$V_{BC} + V_{CE} + V_{EB} = 0$$

$$V_{BC} + 4V_B - V_B = 0$$

$$\Rightarrow V_{BC} = -3V_B$$

As long as we find V_B , we know V_{BC} .

$$V_B = 6i = 6 \cdot \frac{2.5}{2} = 7.5 \text{ V}$$

$$\therefore V_{BC} = -22.5 \text{ (V)}$$